


POJEMNOŚĆ ZASTĘPCZA KONDENSATORÓW. KARTA PRACY

Imię i nazwisko

Klasa

Data

Zadanie 1

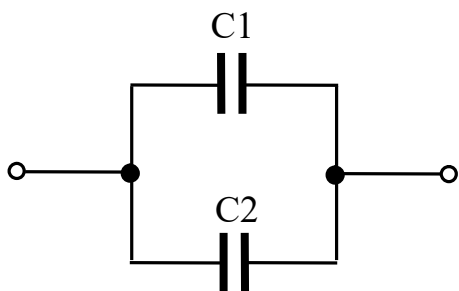

$$C_1 = 8 \text{ pF}$$

$$C_2 = 5 \text{ pF}$$

$$C_z = ?$$

Zadanie 2




$$C_1 = 10 \text{ nF}$$

$$C_2 = 20 \text{ nF}$$

$$C_z = ?$$

Zadanie 3

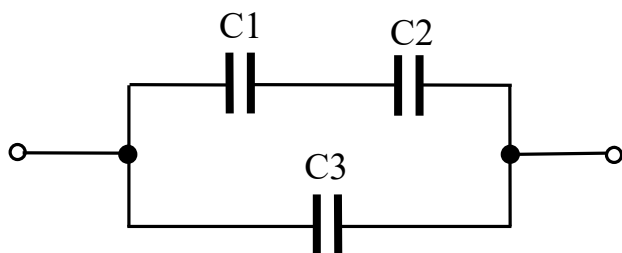


$$C_1 = 3 \text{ } \mu\text{F}$$

$$C_2 = 6 \text{ } \mu\text{F}$$

$$C_3 = 7 \text{ } \mu\text{F}$$

$$C_z = ?$$

Zadanie 4

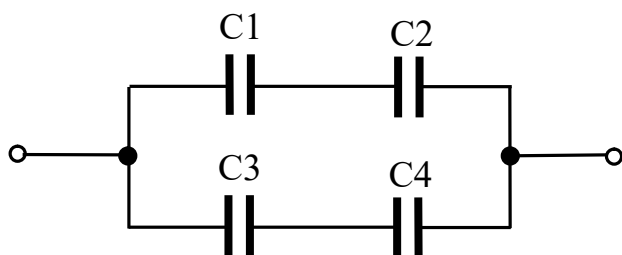

$$C_1 = 3 \text{ } \mu\text{F}$$


$$C_2 = 6 \text{ } \mu\text{F}$$

$$C_3 = 7 \text{ } \mu\text{F}$$

$$C_4 = 5 \text{ } \mu\text{F}$$

$$C_z = ?$$

Zadanie 5

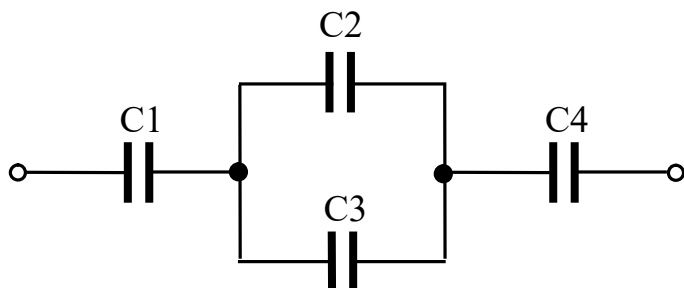

$$C_1 = 3 \text{ F}$$

$$C_2 = 6 \text{ F}$$

$$C_3 = 9 \text{ F}$$

$$C_4 = 5 \text{ F}$$

$$C_z = ?$$